

Seat No.	
----------	--

Set	P
-----	---

**B.Sc. (E.C.S.) (Semester - I) (NEP CBCS) Examination:
March/April – 2026
Digital Electronics and Microprocessors (G06-0103)**

Day & Date: Wednesday, 29-04-2026
Time: 12:00 PM To 01:30 PM

Max. Marks: 30

Instructions: 1) All questions are compulsory.
2) Figures to the right indicate full marks.

Q.1 Choose the correct alternative.

06

- 1) AND gate is _____.
a) A/B
b) $A-B$
c) $A+B$
d) $A.B$
- 2) A J-K flip-flop made to toggle _____.
a) $J = 0, K = 0$
b) $J = 1, K = 0$
c) $J = 0, K = 1$
d) $J = 1, K = 1$
- 3) _____ are universal gates.
a) NOT
b) NAND & NOR
c) AND
d) NOT, AND, & OR
- 4) 8085 is _____ bit microprocessor.
a) 8 bit
b) 16 bit
c) 32 bit
d) 4 bit
- 5) _____ is branch control group of instruction.
a) MOV
b) ADD
c) CALL
d) RAR
- 6) Address bus of 8085 is _____ bit.
a) 8 bit
b) 16 bit
c) 32 bit
d) 4 bit

Q.2 Answer the following. (Any Three)

06

- Define logic gates.
- Explain D flip-flop.
- Draw symbol of AND, OR, NOT and EX-OR.
- List data transfer group of instructions.
- Define Machine cycle and instruction cycle.

- Q.3 Answer the following. (Any Two) 06**
- a) Write features of 8085.
 - b) Explain Half Adder.
 - c) Explain 4:1 multiplexer.
- Q.4 Answer the following. (Any Two) 06**
- a) Explain system bus architecture of 8085.
 - b) Write a program for 8 bit Addition.
 - c) Explain RS flip-flop.
- Q.5 Answer the following. (Any One) 06**
- a) Explain Pin diagram of 8085.
 - b) Explain Full adder with suitable diagram.